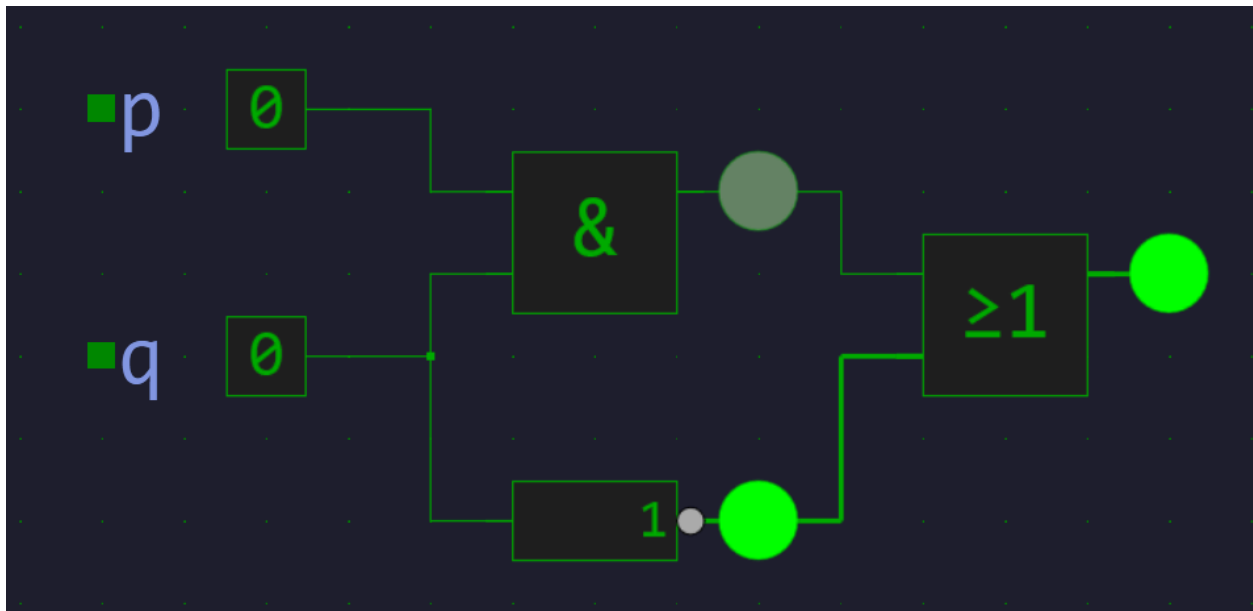


Tablas de verdad - Leonardo Torres


Circuito 1

p	q	p AND q	NOT q	(p AND q) OR (NOT q)
V	V	V	F	V
V	F	F	V	V
F	V	F	F	F
F	F	F	V	V




Circuito 2

p	q	p OR q	NOT (p OR q)	NOT (p OR q) AND (p OR q)
V	V	V	F	F
V	F	V	F	F
F	V	V	F	F
F	F	F	V	F

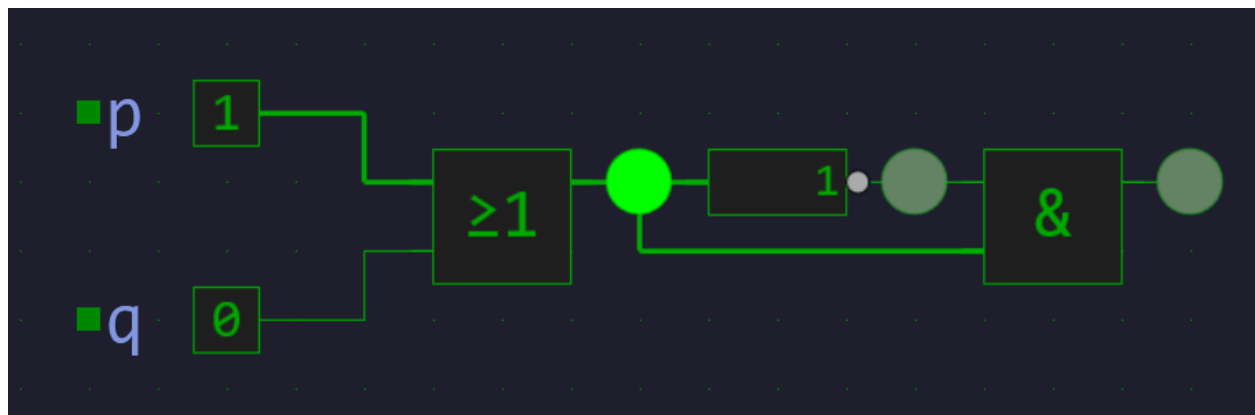

Circuito 3

$p \ q$	$p \text{ OR } q$	$(p \text{ OR } q) \text{ AND } q$	$\text{NOT } q$	$[(p \text{ OR } q) \text{ AND } q] \text{ OR } (\text{NOT } q)$
V V	V	V	F	V
V F	V	F	V	V
F V	V	V	F	V
F F	F	F	V	V

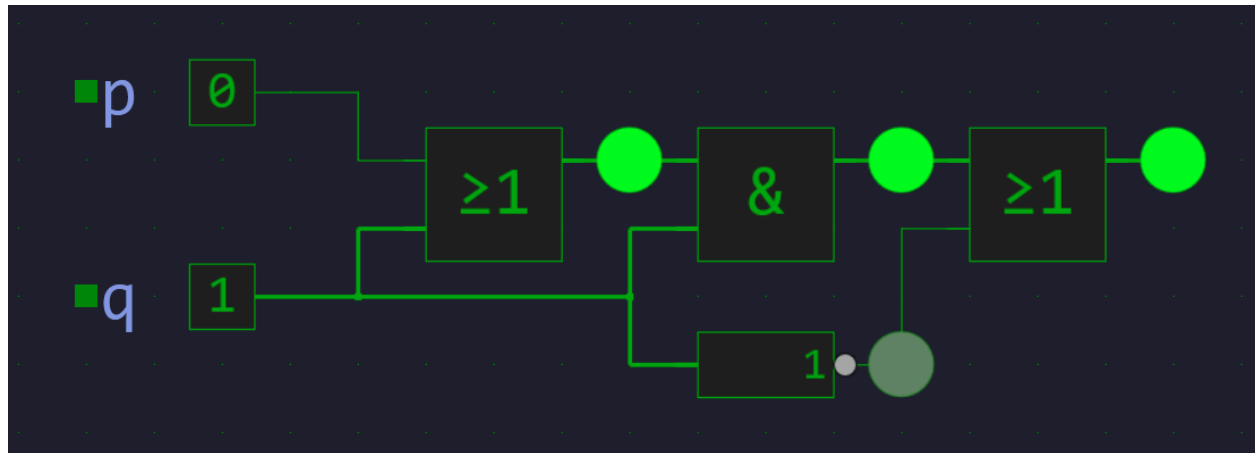

Circuito 4:

p q	p OR q	(p OR q) AND q	NOT q	[(p OR q) AND q] AND (NOT q)
V V	V	V	F	F
V F	V	F	V	F
F V	V	V	F	F
F F	F	F	V	F

